

# Lab 5 Preparation

1

## Lab 5 Components

- Part I: Create a counter
  - Use the synchronized counter circuit described in lectures.
- Part II: Slow down the clock
  - Use the counter and the on-board clock to create a slower clock.
- Part III: Morse code decoder
  - Decode incoming Morse Code signals!
  - Uses code from Part II ☺

2

## Design Guidelines

- A note on `always` blocks:
  - Combinational Circuits use blocking assignment statements (the `=` operator)
  - Sequential Circuits use non-blocking assignment statements (the `<=` operator)


```
always @(*) begin
  q = d;
end
```

```
always @(posedge clock) begin
  q <= d;
end
```

- Do NOT mix assignment types in the same `always` block!

3

## Part I – 4-bit Counter

 

- Diagram shows a 4-bit synchronous counter, made with T flip-flops
  - The T flip-flops here have an active-low asynchronous reset (`Clear_b`).
- Need to use hierarchical design to make an 8-bit counter.

4

## Part I (continued)

- Prelab parts:
  - Draw and label 8-bit counter schematic.
  - Write Verilog code for flip-flop and counter
    - Don't use "tff" as a module name.
  - Simulate your counter to confirm correctness.
  - Augment Verilog code with input/output layer.
  - Analyze your design!
    - Logic Utilization (in ALMs)
    - Maximum Frequency ( $F_{max}$ )
    - Netlist Viewer

} Tools in  
Quartus

5

## Part II: More Counters

- Main goal:
  - Display incrementing digits on a hex display at different speeds (e.g., once per second, twice per second, etc)
- How do we do this?
  1. Need access to a clock signal.
  2. Need to adjust this clock signal to the right speed.
  3. Need to increment a counter at this adjusted clock speed.

6


## Part II (continued)

- Step #1: Finding a clock signal
  - DE1-SoC has a 50MHz clock
    - Pin `CLOCK_50`
  - Hertz (Hz) => number of cycles per second
    - 50MHz => How many clock cycles per second?
    - Would you be able to see that?

7
 
## Part II (continued)

- Step #2: Slowing down the clock.
  - Load a counter with a countdown value (through a parallel load) and produce an enable signal when the countdown reaches zero.



- Another module will use this enable signal to determine whether it will change on the next clock pulse or not.

8

## Part II: An Aside

- Here is an alternate implementation of counters:

```
reg [3:0] q;


always @(posedge clock)
begin
    if (Clear_b == 1'b0)
        q <= 0;
    else
        q <= q + 1;
end
```

- Things to note:
  - Non-blocking assignment (sequential circuit)
    - Means that assignments are implemented in parallel, not series.
  - Synchronous active-low Clear signal

9
 
## Part II (cont'd)

- Step #3: Updating the display counter.
  - You will need 2 counters for this:
    - A RateDivider counter (from previous step)
    - A Display counter (that feeds to the 7-segment decoder)
    - Both will be synchronized to the same 50MHz clock.



- Recall the purpose of an Enable signal in a counter.
  - How often do you want the Display counter to increment?
  - SW[1] and SW[0] will control that rate.

10

## Part III – Morse Code


- Morse Code: "A method of transmitting text information as a series of on-off tones, lights, or clicks that can be directly understood by a skilled listener or observer without special equipment."

S	...
T	—
U	...—
V	...—
W	—...—
X	—...—
Y	—...—
Z	—...—

11
 
## Part III (continued)

- You will be transmitting individual letters using a single red LED
  - Dot => 0.5 seconds LED on
  - Dash => 3 \* 0.5 seconds LED on
  - Pause (between symbols or in the end of transmission) => 0.5 seconds LED off



12

## Part III (continued)

- How do you do this?
  - Step #1: Create a LookupTable (LUT)
    - Switch values as input, binary representation of the corresponding Morse code letter to transmit as output.
  - Step #2: Create a shift register
    - When the KEY input sends a signal, load a shift register with the current value from the lookup table.
    - Shift out a bit on each clock cycle and send it to the LED.

13


## Part III (continued)

- How to decide on the binary representation in the LUT
  - Each bit corresponds to 0.5 seconds of light (1) or no light (0).
  - Example: • – (“dot dash”)
    - Multiple ways this could be represented:
      - 101110
      - 10001110
      - 10111000
      - 10011100000000
  - All of these look like “dot dash” in the end, so it’s up to you (or up to the longest letter you encode)
- How do you make the shift register move bits out every half a second?
  - Rate divider from Part II ☺

14

## Part III (continued)

- How it all comes together:

 

15