 


# Lab 2 Preparation


## Lab 2

- Using the DE1-SoC
- Creating a project using Quartus Prime.
- Intro to Verilog.
- Lab2 Topics
  - Multiplexers, Hierarchy, Decoders, 7-segment displays



2

## Meet the DE1-SoC board!

 

3


## Meet the DE1-SoC board!

- It's a System On a Chip (SoC) w/
  - Altera's Cyclone® V 5CSEMA5F31 FPGA, and
  - a Dual-core ARM Cortex-A9 hard processor (HPS)
- 64 MB SDRAM on FPGA device
- Six 7-segment displays
- 10 toggle switches
- 10 LEDs
- 9 green LEDs
- Four pushbutton switches

4
 
## What does that mean?

- Key term: FPGA.
  - Stands for Field Programmable Gate Array.
  - A regular network of logic that can be programmed and reprogrammed to implement any circuit.
  - Circuits aren't build by hand from now on; they're programmed using languages like Verilog or VHDL.



5

## Quartus Prime

- Tool provided by Altera that compiles Verilog programs, and uploads the result to the FPGA.
- When you do your lab, login at the lab computers with your UTORid.
  - Make sure you've activated your ECF account.
- Quartus Prime should be available from the start menu. You should use Quartus 18.1.



6

## Quartus Prime (cont'd)

- How to create projects for the lab:
  1. Create a new Quartus Prime project for your circuit. Select Cyclone V 5CSEMA5F31C6 as the target chip, which is the FPGA chip on the Altera DE1-SoC board.
  2. Create a Verilog module for the current part of the lab and include it in your project.
  3. Include in your project the required pin assignments for the DE1-SoC board, as discussed above. Compile the project.
    - The "play" icon in the menu bar.
  4. Download the compiled circuit into the FPGA chip.
    - Click the icon with the ribbon cable on the menu bar.

7

## Intro to Verilog

- Verilog is a hardware description language (HDL) that is used to specify a circuit design.
- Instead of specifying actual gate connections, Verilog takes in more high-level functionality, which is translated into digital logic before implementing it on the hardware.

8

## Learning about Verilog

```

monitor dm
reg a b c;
initial begin : a_b
$monitor ("DM: a: %d b: %d", $time, a, b);
wait;
a <- 0; b <- 0;
c <- 1;
wait;
a <- 1; b <- 0;
c <- 1;
wait;
a <- 0; b <- 1;
c <- 1;
wait;
a <- 1; b <- 1;
c <- 0;
$monitor;
end // a_b

initial begin : extra
$monitor ("DM: a: %d", $time, a);
$monitor ("DM: b: %d", $time, b);
end // extra

always @(*) begin : alu_strobe
$strobe ("DM: SW STROBE ALWAYS: a: %d b: %d c: %d", $time, a, b, c);
end //

always @(*) begin : al
$display ("DM: SW ALWAYS: a: %d b: %d c: %d", $time, a, b, c);
end // al

```

9

## Creating Verilog: XOR gates

- XOR gates have high output when the inputs are different, and low output when the inputs are the same.



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

- Could we make this from AND, OR and NOT gates?

10

## Creating Verilog: XOR gates

```

module xor(Y,A,B);
    output Y;
    input A, B;
    wire not_A, not_B;
    wire A_and_notB, B_and_notA;
    not n1(not_A, A);
    not n2(not_B, B);
    and a1(A_and_notB, A, not_B);
    and a2(B_and_notA, B, not_A);
    or o1(Y, A_and_notB, B_and_notA);
endmodule

```

11

## A sample Verilog program

```

// Simple module that connects the
// SW switches to the LEDR lights
1 module part0 (SW, LEDR);
2     input [9:0] SW;           // toggle switches
3     output [9:0] LEDR;       // red LEDs
4
5     assign LEDR[9:0] = SW[9:0];
endmodule

```

- This is a basic Verilog module that:
  - specifies the ports that will be used (line 1),
  - designates how many will be used for input (line 2) and for output (line 3)
  - Specifies the logic that will take place within the module (line 4)

12

## Things to note

- The name of the module should be the same as the high-level line that says "module XXX (...)".
- The ports can be input, output and inout (focus on the first two).
- The assign keyword.
- The square brackets indicate a vector of values. Individual bits within that vector can be read or assigned using usual array notation (e.g. LED[0] = SW[0] or LED[2:0] = SW[2:0]).
- Don't forget the semicolons after each statement!

13

## Wires in Verilog

- The first declaration is for a single wire, while the second indicates a vector.

```
// The following lines create
// intermediate wires.
wire Sel;
wire [7:0] X, Y, M;
```

14

## To Be Continued Next Week

- Next week, we'll write a module in Verilog and do an in-class demo.
- The next slide (operators) is provided for future reference. Each lab handout introduces you to the operators you'll need.

15

## Operators


- Signals can be combined together in all the usual ways, and some new ones that are specific to digital values.

Operator Type	Operator Symbol	Operation Performed
Arithmetic	*	Multiply
	/	Division
	+	Add
	-	Subtract
	%	Modulus
	++	Unary plus
Logical	~	Unary minus
	!	Logical negation
	&&	Logical and
Relational		Logical or
	>	Greater than
	<	Less than
Equality	>=	Greater than or equal
	<=	Less than or equal
	==	Equality
Reduction	!=	Inequality
	~	Bitwise negation
	~&	nand
Shift		or
	~	nor
	^	xor
Concatenation	^~	xnor
	~^	xnor
	>>	Right shift
Conditional	<<	Left shift
	[]	Concatenation
	?	conditional

16

## Multiplexers

- All you need to know:

 


s <sub>1</sub>	s <sub>0</sub>	Y
0	0	U
0	1	V
1	0	W
1	1	X

17
 
## Using 7-segment displays

The DE1-SoC board has six 7-segment displays. These displays are arranged into three pairs, meant for displaying numbers of various sizes. As indicated in the schematic in Figure 3-17, the seven segments (common anode) are connected to pins on Cyclone V SoC FPGA. Applying a low logic level to a segment will light it up and applying a high logic level turns it off.


Each segment in a display is identified by an index from 0 to 6, with the positions given in Figure 3-17. Table 3-9 shows the assignments of FPGA pins to the 7-segment displays.



18
 
## How HEX segments work

- HEX segments are "active low", meaning that they turn on when their input signal is 0, not 1.
  - If you set HEXo[0] to 1, there is no voltage drop across the segment, so it doesn't turn on.
  - If you set HEXo[0] to 0, the voltage drop across the segment makes current flow, causing it to turn on.




19

## Activating HEX displays

- Need to set segment 0 (top segment) **low** in the following input cases:

- 0000 -- "0"
- 0010 -- "2"
- 0011 -- "3"
- 0101 -- "5"
- 0110 -- "6"
- 0111 -- "7"
- 1000 -- "8"
- 1001 -- "9"
- 1010 -- "A"
- 1100 -- "C"
- 1110 -- "E"
- 1111 -- "F"

- How do we express this?

 


20
 
## Activating HEX displays

- Could also set segment 0 (top segment) **high** in the other input cases:

- 0001 -- "1"
- 0100 -- "4"
- 1011 -- "B"
- 1101 -- "D"



- Can be expressed as a four-part Boolean expression:

```
HEX[0] = ~SW[3] & ~SW[2] & ~SW[1] & SW[0] |
~SW[3] & SW[2] & ~SW[1] & ~SW[0] |
SW[3] & ~SW[2] & SW[1] & SW[0] |
SW[3] & SW[2] & ~SW[1] & SW[0];
```

21

## Activating HEX displays


```
HEX[0] = ~SW[3] & ~SW[2] & ~SW[1] & SW[0] |
~SW[3] & SW[2] & ~SW[1] & ~SW[0] |
SW[3] & ~SW[2] & SW[1] & SW[0] |
SW[3] & SW[2] & ~SW[1] & SW[0];
```

- Can this be reduced any further?
  - ...sadly, no ☹
- How do we know?
  - Karnaugh maps!

22
 
## Activating HEX displays

- Can you write the expressions for HEX[1] to HEX[6]?
- Can you reduce these expressions to the simplest gate form?



23

## Pin assignments

- Before you start using values like SW[0] or HEX0[0], you need to import a pin assignment file that associates the pin numbers on the chip (PIN\_AB12, PIN\_AC12, PIN\_V16) with more intuitive labels (SW[0], SW[1], LEDR[0], etc).
- In Quartus, select *Assignments* → *Import Assignments*
  - The DE1\_SoC.qsf file (posted on Canvas) associates signal names to pins on the chip so you can refer to them in your design.

24

## Some Verilog References

- Check out the Verilog Primer and other resources on Quercus for more information on the Verilog language.
- ECE also provides reference documentation for the lab rooms at:
  - <http://www-ug.eecg.utoronto.ca/des/>