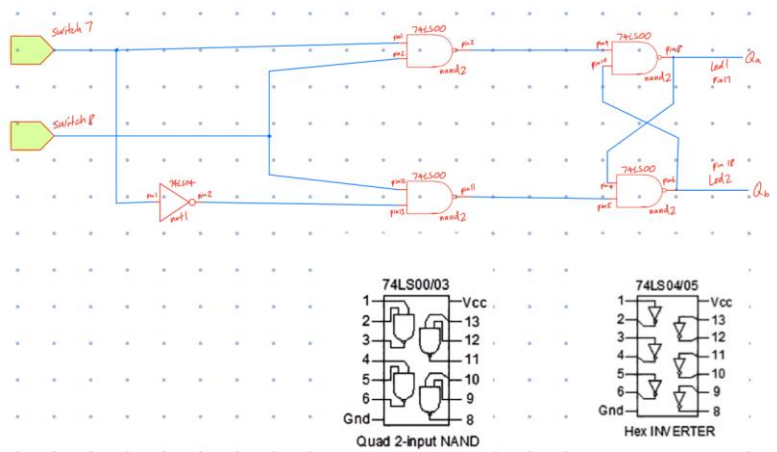


Part I:



Digital Board Header Pin Assignment			
Pin#	Description	Description	Pin#
1	Switch #1	Switch #2	2
3	Switch #3	Switch #4	4
5	Switch #5	Switch #6	6
7	Switch #7	Switch #8	8
9	Ground	NC	10
11	Ground	NC	12
13	Ground	NC	14
15	Ground	NC	16
17	LED #1	LED #2	18
19	LED #3	LED #4	20
21	LED #5	LED #6	22
23	LED #7	LED #8	24
25	Ground	NC	26
27	Ground	NC	28
29	Ground	NC	30
31	Ground	NC	32
33	Clock	NC	34
35	NC	NC	36
37	NC	Pulse Button	38
39	NC	NC	40


Figure 4: Digital board header pin assignment

1. Schematic of gated D latch labelled with connecting pins and outputs.

4. No, a gated D latch does not experience the issue of indeterminate states, so if the outputs are not fed back into any of the inputs, any combination of Clk and D can be tested. However, it needs to be noted that clk needs to be high for a change in output to be seen. So initial testing should not be done when clk is at 0.

Part II:

 
1. Verilog and test code submitted on Quercus.




2. Modelsim simulation for ALU register over various inputs. We can see that the reg_out trails ALUout by 5 ns when the reset_n value is high, as expected. Other inputs behave as expected.

Part III:

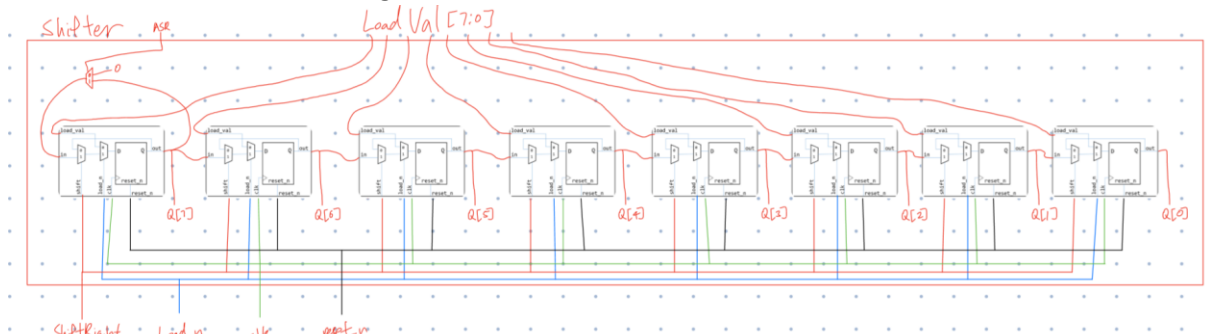1. As no values are loaded and nothing is being shifted, the shift register should display a constant 8'b00000000, meaning all the LED's should be off.



 2. Schematic of the 8-bit shifter.
3. Code for 1 bit shifter included in shifter.v code as shiftbit module and submitted on Quercus.
4. Code for 8 bit shifter included as top module shifter in shifter.v code submitted on Quercus.



5. Simulation done with shifter with both leading 1 and leading 0 inputs and tested on both ASR and non-ASR shifts. Outputs work as expected.