

2. Resetn is a synchronous active low signal. To reset the FSM, force resetn to be 0.
3. Code submitted on Quercus.

[illegible]

Simulation for 1111 and 1101 inputs, we can see that the output LED goes high for both.


Part II:

2.

$F_n$	<i>out</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>x</i>	<i>r</i>	<i>sa</i>	<i>sb</i>	<i>op</i>	<i>go</i>	$F_{n+1}$
S_LOAD_A	0	1	0	0	0	0	00	00	0	0	S_LOAD_A
S_LOAD_A	0	1	0	0	0	0	00	00	0	1	S_LOAD_A_WAIT
S_LOAD_A_WAIT	0	1	0	0	0	0	00	00	0	0	S_LOAD_B
S_LOAD_A_WAIT	0	1	0	0	0	0	00	00	0	1	S_LOAD_A_WAIT
S_LOAD_B	0	0	1	0	0	0	00	00	0	0	S_LOAD_B
S_LOAD_B	0	0	1	0	0	0	00	00	0	1	S_LOAD_B_WAIT
S_LOAD_B_WAIT	0	0	1	0	0	0	00	00	0	0	S_LOAD_C
S_LOAD_B_WAIT	0	0	1	0	0	0	00	00	0	1	S_LOAD_B_WAIT
S_LOAD_C	0	0	0	1	0	0	00	00	0	0	S_LOAD_C
S_LOAD_C	0	0	0	1	0	0	00	00	0	1	S_LOAD_C_WAIT
S_LOAD_C_WAIT	0	0	0	1	0	0	00	00	0	0	S_LOAD_X
S_LOAD_C_WAIT	0	0	0	1	0	0	00	00	0	1	S_LOAD_C_WAIT
S_LOAD_X	0	0	0	0	1	0	00	00	0	0	S_LOAD_X
S_LOAD_X	0	0	0	0	1	0	00	00	0	1	S_LOAD_X_WAIT
S_LOAD_X_WAIT	0	0	0	0	1	0	00	00	0	0	S_CYCLE_0
S_LOAD_X_WAIT	0	0	0	0	1	0	00	00	0	1	S_LOAD_X_WAIT
S_CYCLE_0	1	1	0	0	0	0	00	11	1	0	S_CYCLE_1
S_CYCLE_0	1	1	0	0	0	0	00	11	1	1	S_CYCLE_1
S_CYCLE_1	1	1	0	0	0	0	00	11	1	0	S_CYCLE_2
S_CYCLE_1	1	1	0	0	0	0	00	11	1	1	S_CYCLE_2
S_CYCLE_2	1	1	0	0	0	0	01	11	1	0	S_CYCLE_3
S_CYCLE_2	1	1	0	0	0	0	01	11	1	1	S_CYCLE_3
S_CYCLE_3	1	1	0	0	0	0	00	10	0	0	S_CYCLE_4
S_CYCLE_3	1	1	0	0	0	0	00	10	0	1	S_CYCLE_4
S_CYCLE_4	0	0	0	0	0	1	00	01	0	0	S_LOAD_A
S_CYCLE_4	0	0	0	0	0	1	00	01	0	1	S_LOAD_A

State table for new computation.


3.

 

State diagram.


4. Verilog code submitted on Quercus.

5.

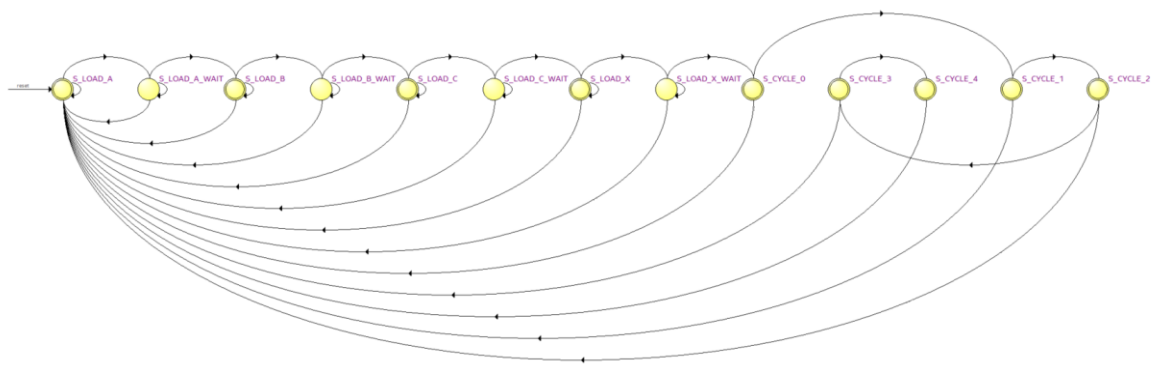

Generated FSM.

6.

 

Modelsim tests, with A = 2, B = 3, C = 4, x = 5, output 117

