

Lab 3 Tutorial

Exploring Verilog


- Verilog can express logic beyond the basic gate-by-gate specification.
 - Typically in `always` blocks
- Example: `case` statements
 - Not the same as case statements in other languages!
 - **case** statements in Verilog provide output behaviour for all possible input values
 - Like specifying the output for all minterm cases
 - How would you do a multiplexer with this?

Part 1: Mux + case statement

- Use `case` statement and `always` block to implement a 7-to-1 multiplexer.
 - See the example of a `hex_decoder` from class.
- Key points:
 - Combination circuits w/ an `always` block.
 - Use `*` in the sensitivity list of your `always` block.
 - Don't forget the `default` case! Or else the tool will need to have memory (which we haven't done yet).
 - New storage term: `reg` (used similar to `wire`)
 - Use `wire` with assignment statement outside `always` blocks, and `reg` within them.

Part 2: Ripple Carry Adders

- Implement a Ripple Carry Adder by connecting (chaining) four full-adders together.
 - Must use hierarchical design!

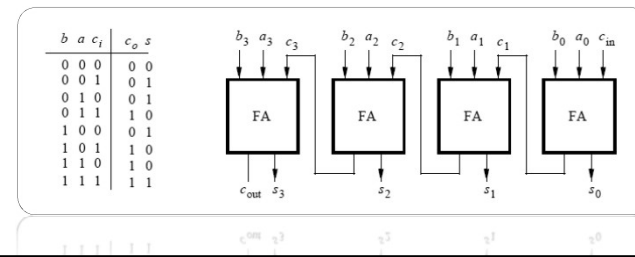

Part 3

- Implement a simple ALU (Arithmetic Logic Unit) and display inputs/outputs to LEDs and 7-segment display (in hex).
 - You should reuse work you did in Lab 2.
 - Uses mux to implement addition, subtraction, inversion, etc.
 - More Verilog operators! ☺

Useful Verilog Operations

Operation Type	Operator Symbol	Operation Performed	Number of Operands
Arithmetic	*	multiply	two
	/	divide	two
	+	add	two
	-	subtract	two
	%	modulo	two
	**	power (exponent)	two
Logical	!	logical negation	one
	&&	logical and	two
		logical or	two
Relational	>	greater than	two
	<	less than	two
	>=	greater than or equal	two
	<=	less than or equal	two
Equality	==	equality	two
	!=	inequality	two
	===	case equality	two
	!==	case inequality	two

Bitwise Operators

- Bitwise Operators (see Table 1 from Lab2)
 - If you use a bitwise operator with two n-bit operands, the result is also an n-bit vector.
- For example:
 - $3'b101 \& 3'b011 \rightarrow 3'b001$
- More general mathematical notation:
 - $(X_{n-1}X_{n-2} \dots X_1X_0 \& Y_{n-1}Y_{n-2} \dots Y_1Y_0)$ results in $W_{n-1}W_{n-2} \dots W_1W_0$ where W_i is $(X_i \& Y_i)$ for every i in $[0, n-1]$.
 - You can use any of these bitwise operators in place of &.

Table 1: Verilog Operators

	bitwise OR
&	bitwise AND
~	bitwise negation
^	bitwise XOR

Reduction Operators

- Reduction Operators have same symbol as bitwise, but
 - they take a single multi-bit operand, and
 - they result in a single-bit vector.
- For example:
 - $(\& 3'b101)$ results in $1'b0$
- General mathematical notation:
 - $(\& X_{n-1}X_{n-2} \dots X_1X_0)$ results in W_0 where W_0 is $(X_{n-1} \& X_{n-2} \& \dots \& X_1 \& X_0)$.
 - Think of this as feeding all n bits of X into a single n-input AND gate with output W_0
 - You can use any of the reduction operators in place of &.

Replication and Concatenation

- The binary value 011 (3 in decimal) is the same as 0011 or 00000011.
 - Adding zeros in the most significant bits of a positive or an unsigned number does NOT change the number being represented!
- Example:
 - If the output of a module is 3-bits and you want to feed it to a 5-bit input of another module, you'd need to use both replication & concatenation!
 - See Background section on Lab3 handout.

More Complex Force Commands

```
force {<signal_name>} <initial value> <initial time>, <new value> <new time>  
-repeat <repeat time> -cancel <cancel time>
```

```
force {a} 0 0, 1 20 -repeat 40  
force {b} 0 0 ns, 1 40 ns -r 80
```

- What's happening here:
 - The waveform for a (see first `force` command) starts low (logic-0) @ 0ns
 - At 20ns, it goes high (changes to logic-1).
 - It stays high until 40ns when this process repeats
 - (i.e., it goes back to 0 until 60ns; at 60ns it goes back to 1 until 80ns and so on..)
 - a is represented by a square wave with a period of 40ns
 - The square waveform for b has double the period of a.
- Don't forget to follow these force commands with a `run` command (e.g., `run 160ns`)!

Specifying a vector:

- What you might want to do:
 - `wire multibit_vector [3:0];`
- The you should do:
 - `wire [3:0] multibit_vector;`
- Additional notes:
 - You can specify a part of this vector's bits (a subset of wires) by writing: `multibit_vector[2:1]`

Frequently asked questions

- Can we use the `2to1mux` module from Lab 2 for prelab Lab3 Part1, or just logic gates?
- Answer:
 - In terms of your Verilog code, you need to use the template provided in page 3 of your Lab 3 handout, i.e., an `always` block with a `case` statement.
 - You should **not** use multiple 2-to-1 muxes like you did in Lab 2. The goal of Part I is to provide you with an alternate way of describing a multiplexer, what we call "behavioural Verilog".
 - The combinational circuit you will describe this way will of course be synthesized using logic gates by Quartus!

Frequently asked questions

- How would one draw a schematic for the mux in Part1?
- Answer:
 - Think of the 7-to-1 mux described in the template as a black box (a building block of your circuit). What will its `MuxSelect` input be connected to? How about the reg `Out`? You need to specify how these are connected to the various FPGA pins.

Frequently asked questions

- Should the default value of the 7 to 1 mux be the same as case 6?
- Answer:
 - It doesn't matter. You can think of the default case as a "don't care" since this is a 7-to-1 mux and not an 8-to-1 mux.
 - That being said, it usually helps with debugging if you hardwire the output of the circuit in that case, as in make it be a known value that does not rely on any of the inputs. For example, making it always be 0 would achieve that.

Frequently asked questions

- When it says that the output should be 1 (8'b00000001) if at least 1 of the 8 bits in the two inputs is 1 using a single OR operation. What do you mean by '*using a single OR operation*'?
- Answer:
 - A '*single OR operation*' is the same as an OR Reduction Operator. Information on reduction operators is available on page 2 of the handout.

Frequently asked questions

- When I try to run my `part3wave.do` on Modelsim I get an error message saying that it cannot find my instantiation of '`ripplecarryadder`' or '`HEXdisplay`'. I have imported these two modules in my project using quartus for Lab3Part3. Do I need to add some lines of code to my `part3wave.do` file to correct this?

Frequently asked questions

- Answer:
 - If the code for these modules is written in separate *.v files you need to specify them in your `vlog` command in ModelSim. What you do in your Quartus project has no effect on ModelSim; notice that we don't even ask you to set-up the Quartus project as part of you prelab.
 - You can specify more than one Verilog files in your `vlog` command; just separate them by spaces:

```
vlog -timescale 1ns/1ns mux.v  
that_other_module_you_used.v a_third_module.v
```

- ModelSim also allows the use of wildcards. For example, assuming you have all the Verilog files you need in the same directory (the one you cd-ed to before running your *.do script), you can simply do:

```
vlog -timescale 1ns/1ns *.v
```